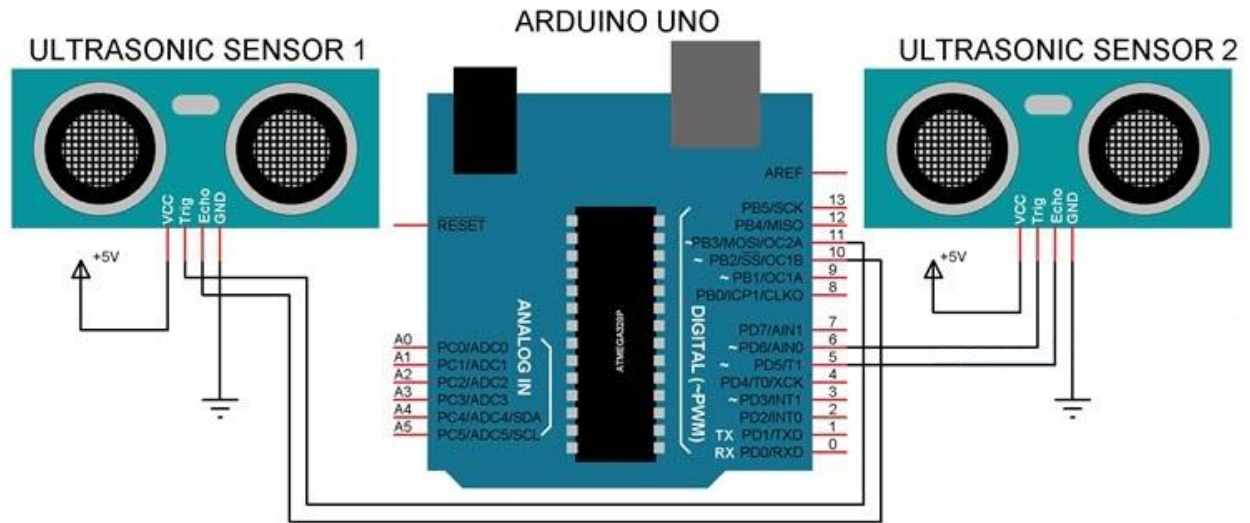


2. FABRICATION OF CIRCUIT



To control the PC with Hand Gestures, just connect the two Ultrasonic sensors with Arduino. We know US sensor work with 5V and hence they are powered by the on board Voltage regulator of Arduino. The Arduino can be connected to the PC/Laptop for powering the module and also for Serial communication. Once the connections are done place them on your monitor as shown below. I have used a double sided tape to stick it on my monitor but you can use your own creativity. After securing it in a place we can proceed with the Programming.

